

Example 50. Determine the voltage drop across the resistor R_1 in the circuit given below with $\mathcal{E} = 60 \text{ V}$, $R_1 = 18 \Omega$, $R_2 = 10 \Omega$.

Solution. As the resistances R_3 and R_4 are in series, their equivalent resistance

$$= 5 + 10 = 15 \Omega.$$

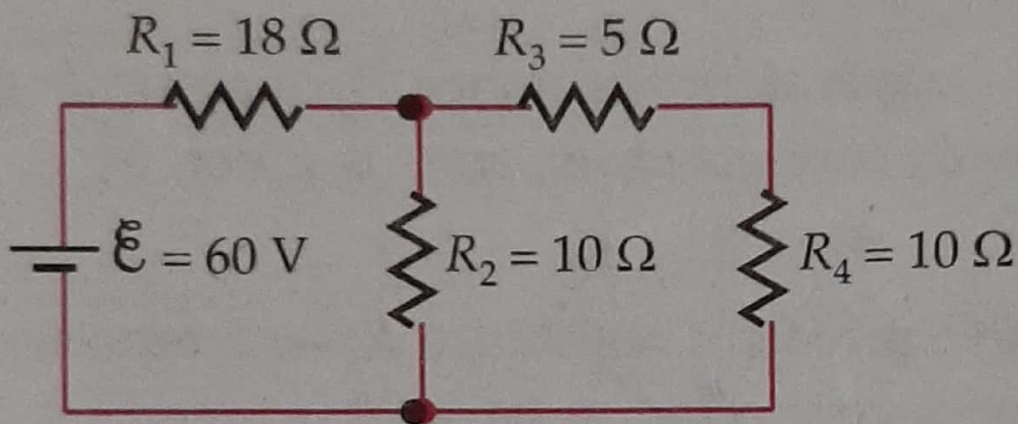


Fig. 3.35

Example 61. Find the effective resistance of the network shown in Fig. 3.41 between the points A and B when (i) the switch S is open (ii) switch S is closed.



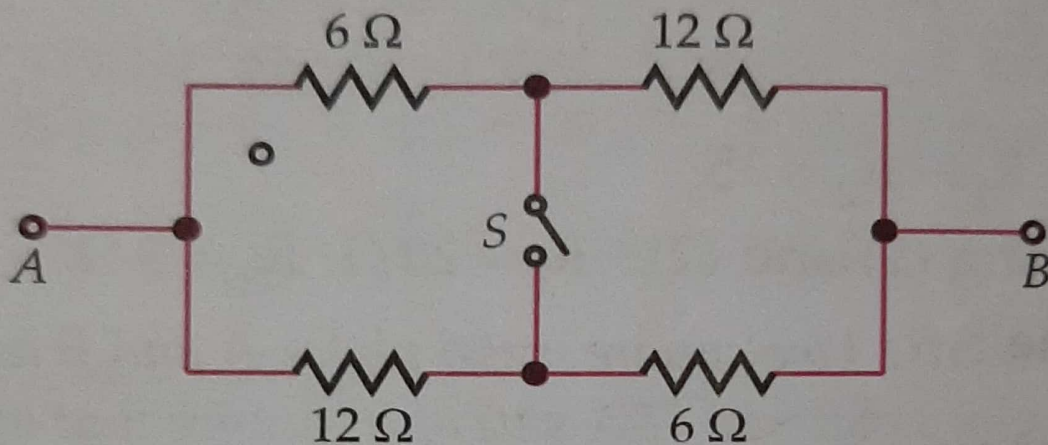


Fig. 3.41

Example 63. In the given circuit, with steady current, calculate the potential difference across the capacitor and the charge stored in it. [CBSE F 17]

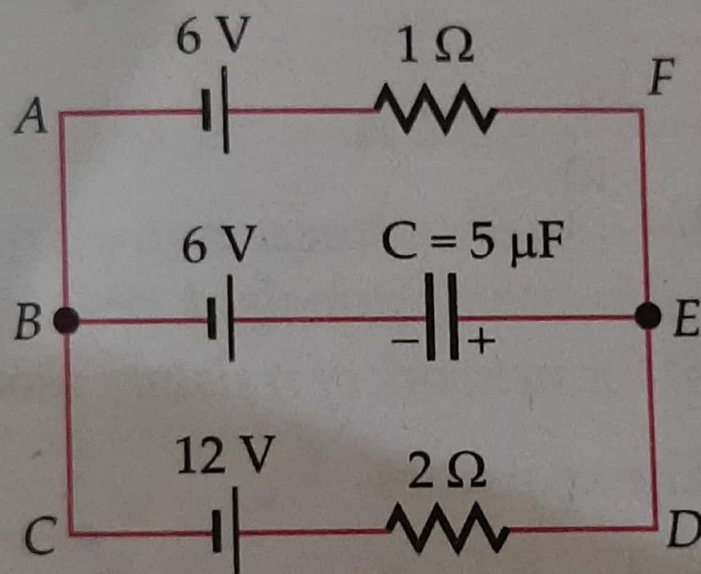

Example 64. In the circuit shown in Fig. 3.45, find the potential difference across the capacitor.

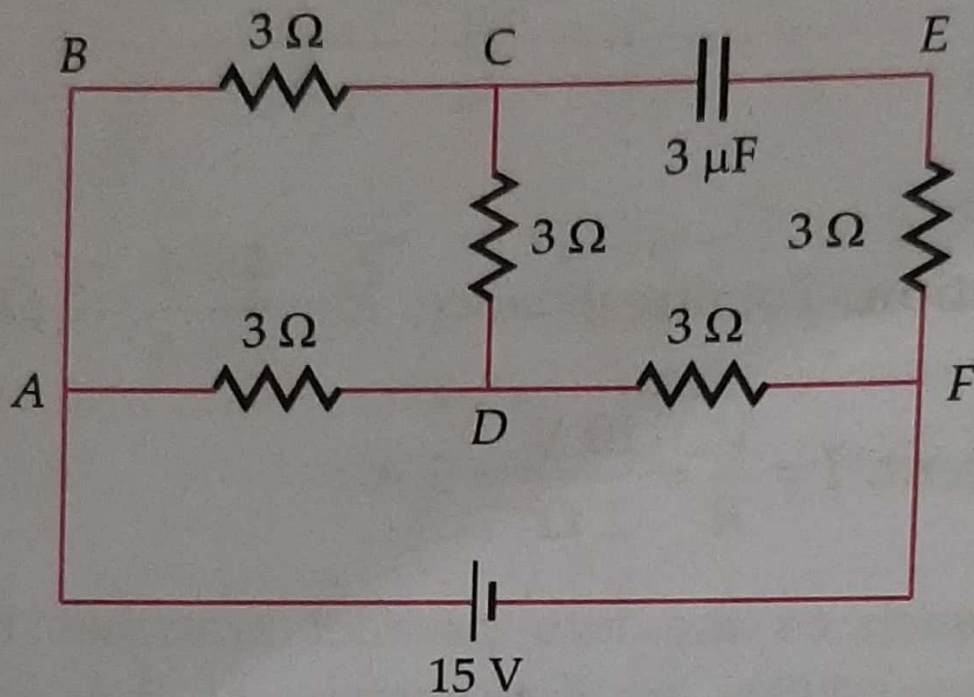

Example 93. In the two electric circuits shown in Fig. 3.117, determine the readings of ideal ammeter (A) and the ideal voltmeter (V). [CBSE D 15C]

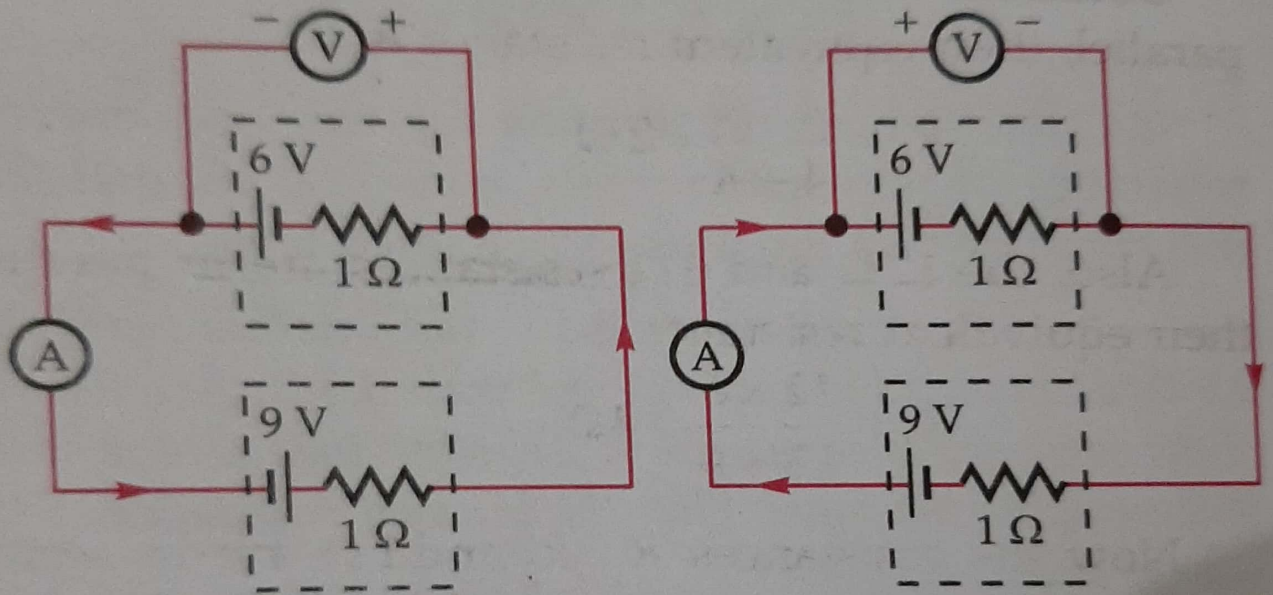


Fig. 3.117

(a)

(b)

Example 91. In the circuit diagram given in Fig. 3.115, the cells E_1 and E_2 have emfs 4 V and 8 V and internal resistances $0.5\ \Omega$ and $1.0\ \Omega$ respectively. Calculate the current in each resistance.

[CBSE D 15C]

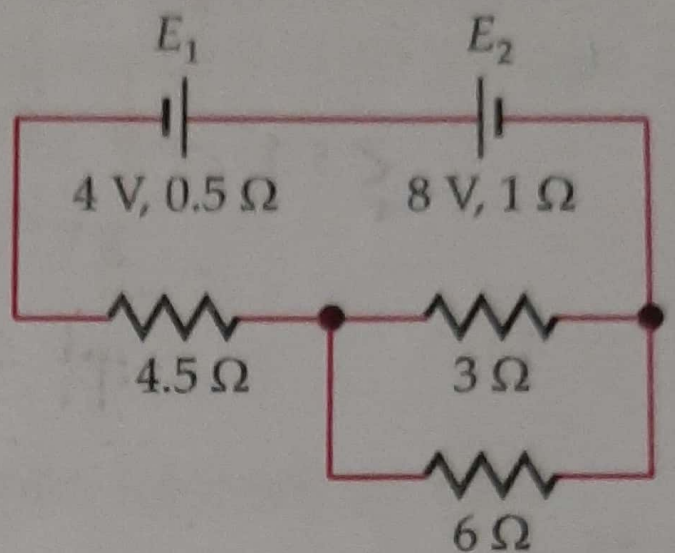


Fig. 3.115

Example 71. Find the equivalent resistance of the circuit shown in Fig. 3.58 between the points A and B. Each resistor has a resistance r .

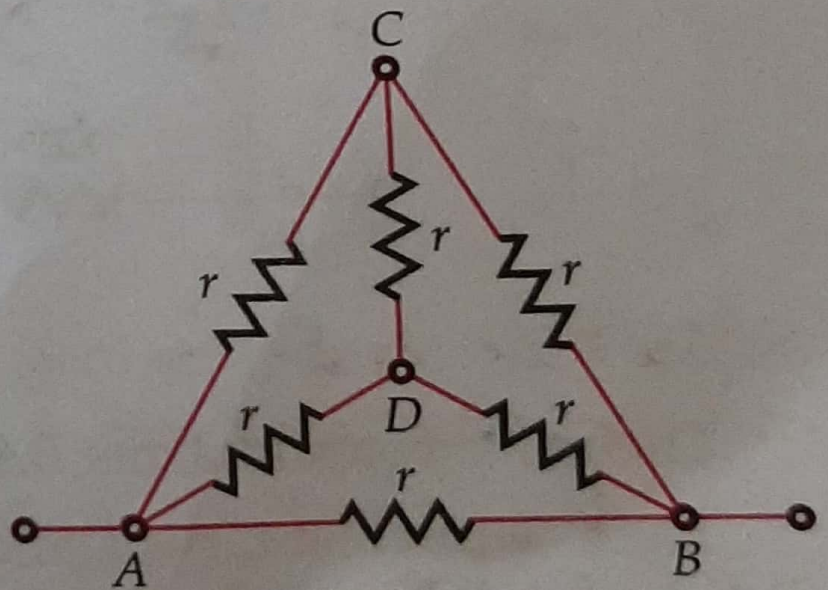


Fig. 3.58